 



# VHDL LANGUAGE

## FLIP-FLOPS, REGISTERS, COUNTERS, AND A SIMPLE PROCESSOR

DR. TIN THET NWEI



# 4-BIT UP COUNTER

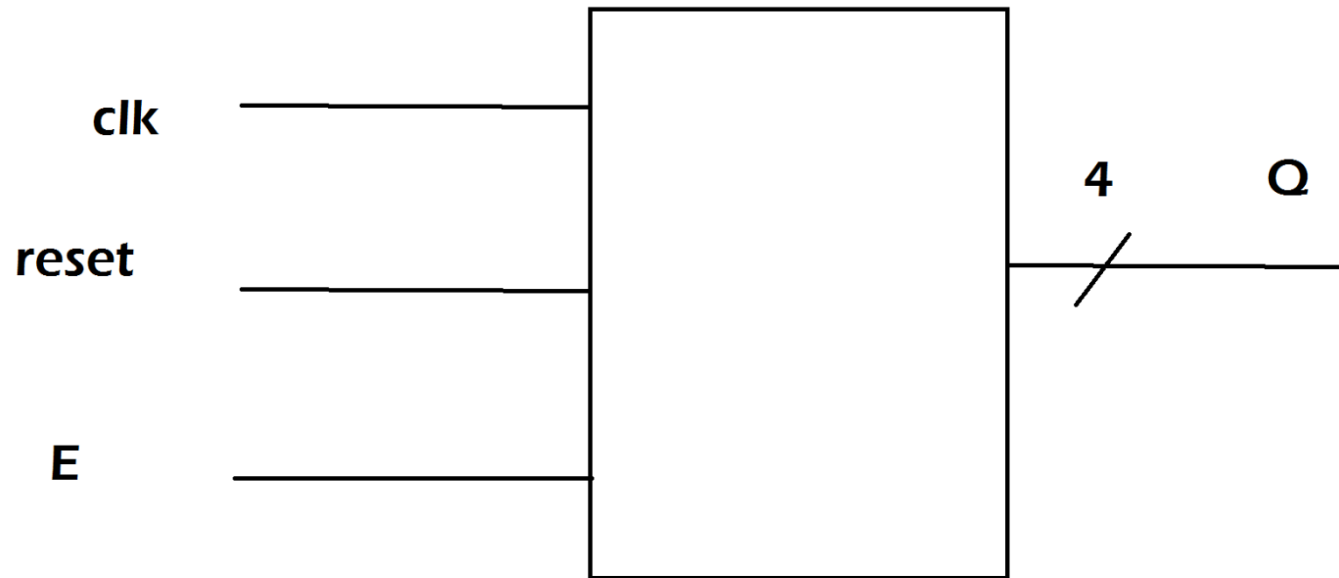

# UP COUNTER


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY upcount IS
    PORT ( Clock, Resetn, E : IN  STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR (3 DOWNT0 0)) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNT0 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

**Figure 7.52** Code for a four-bit up-counter.

# N-BIT UP COUNTER

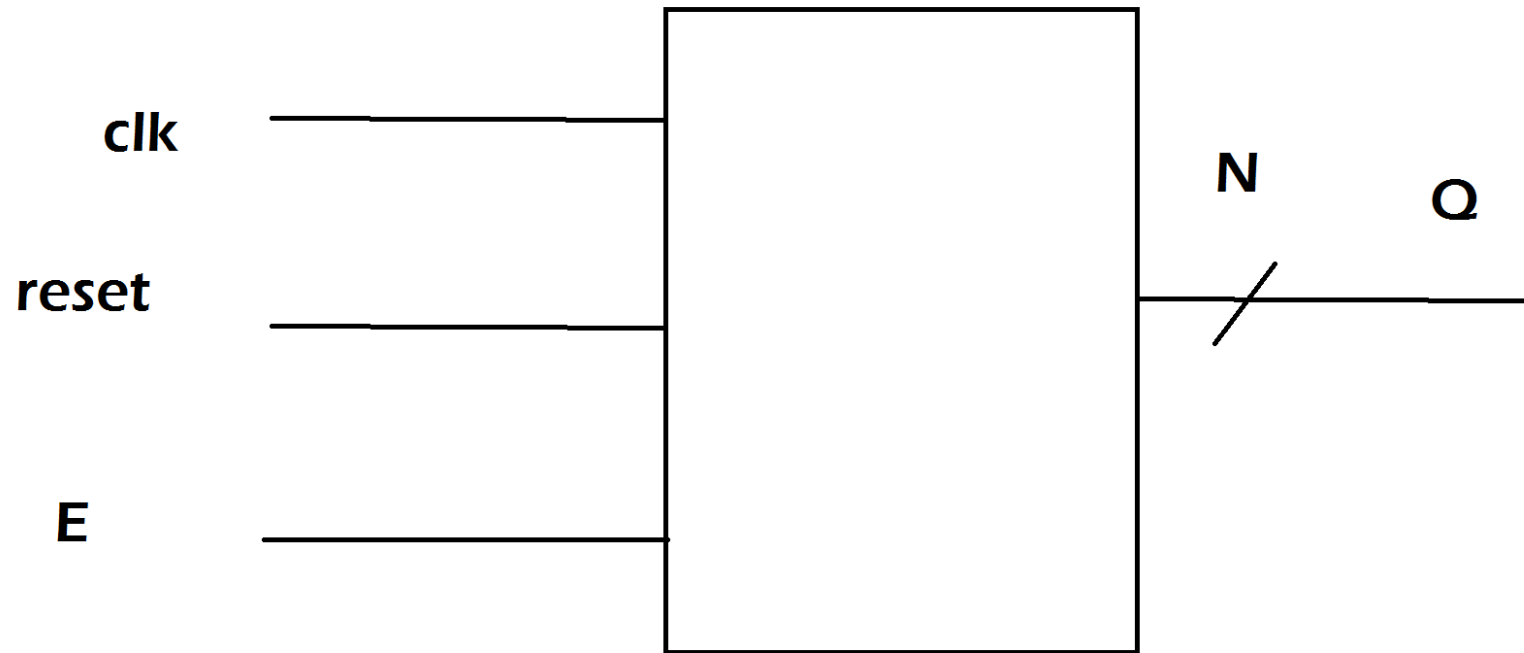

# N-BIT UP COUNTER

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.std_logic_unsigned.all;
```

```
entity n_bit_upcounter is  
  generic ( n:integer:=3);  
  Port ( clk : in STD_LOGIC;  
        En : in STD_LOGIC;  
        reset : in STD_LOGIC;  
        Q : out STD_LOGIC_VECTOR (n downto 0));  
end n_bit_upcounter;
```

```
architecture Behavioral of n_bit_upcounter is  
  signal count : std_logic_vector ( n downto 0);  
begin
```


```
  process ( reset,clk,En )  
  begin  
    if reset ='1' then  
      count<= (others=>'0');  
    elsif rising_edge (clk) then  
      if En ='1' then  
        count<= count+1;  
      else  
        count <= count;  
      end if;  
    end if;  
  end process;
```

```
  Q<= count;  
  
end Behavioral;
```

N=3



N=4

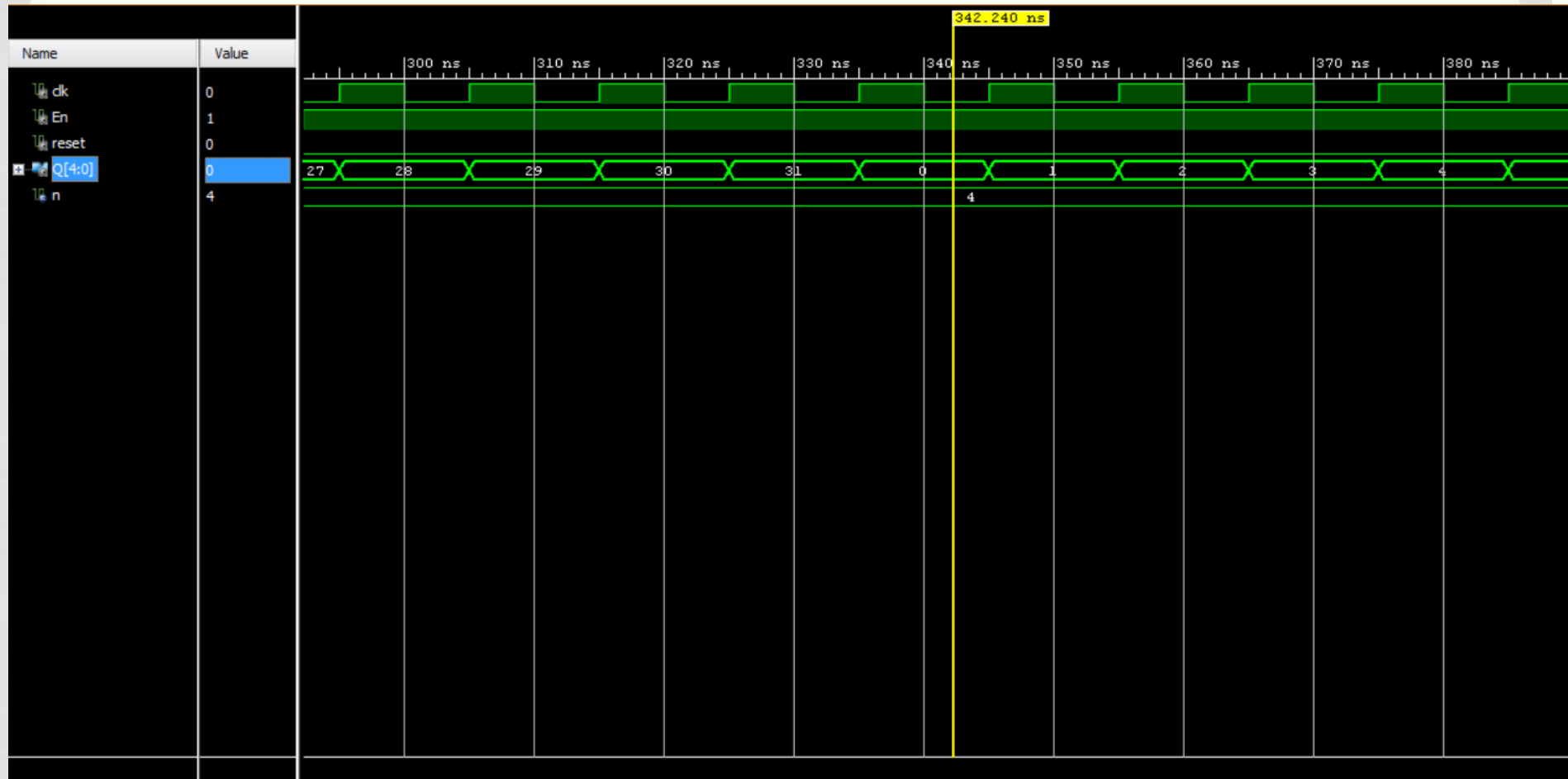

# N-BIT DOWN COUNTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;
entity n_bit_dwn_counter is
    generic ( n:integer:=4);
    Port ( clk : in STD_LOGIC;
          En : in STD_LOGIC;
          reset : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (n downto
0));
end n_bit_dwn_counter;

architecture Behavioral of
n_bit_dwn_counter is
signal count : std_logic_vector ( n downto
0);
```

```
begin
process ( reset,clk,En )
begin
if reset ='1' then
    count<= (others=>'0');
elsif rising_edge (clk) then
    if En ='1' then
        count<= count-1;
    else
        count <= count;
    end if;
end if;
end process;
Q<= count;


end Behavioral;
```




# N-BIT DOWN COUNTER



# N-BIT DOWN COUNTER

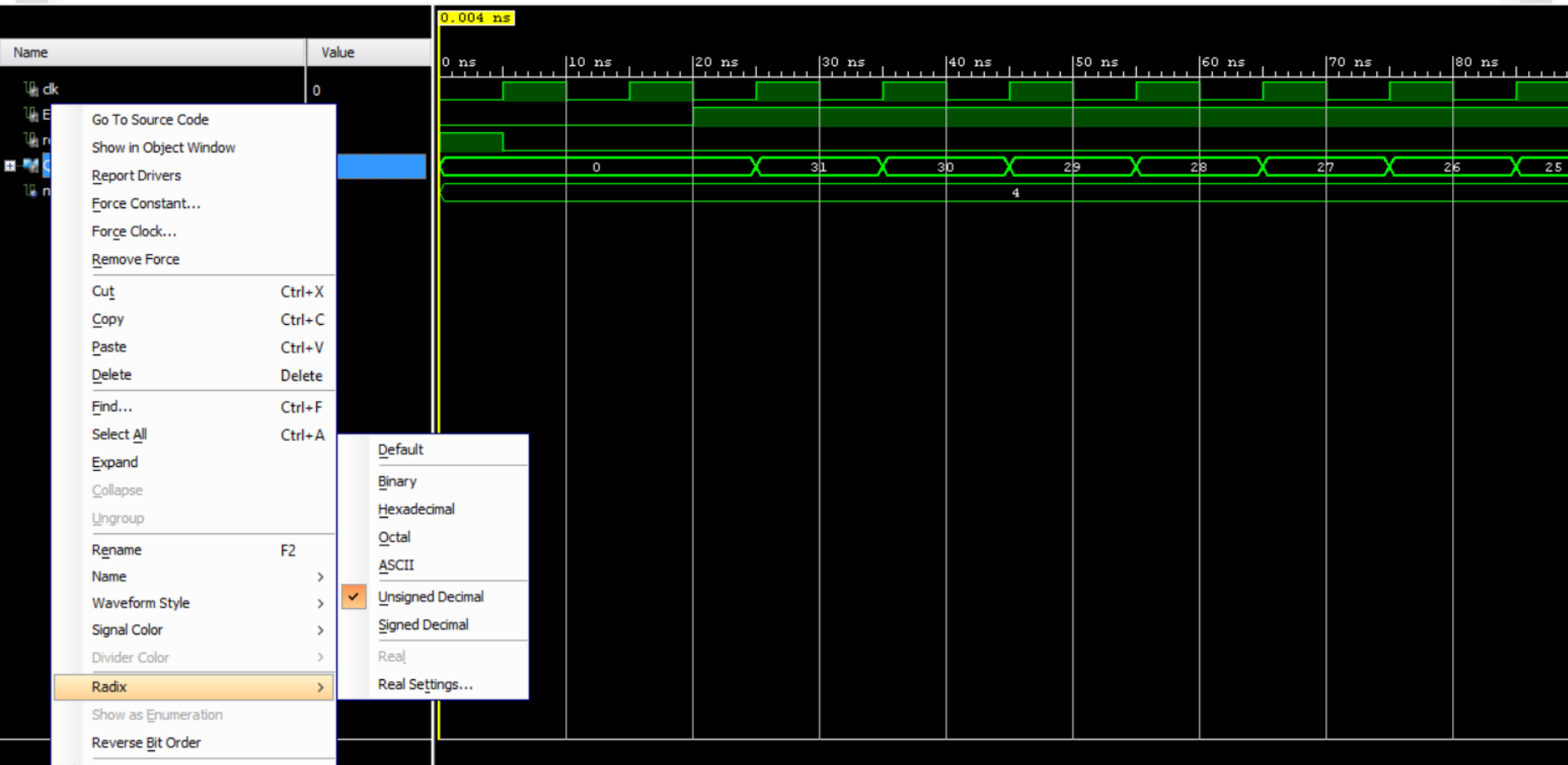

# PARALLEL LOAD UP COUNTER

 

# PARALLEL LOAD UP COUNTER

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity up_counter is
generic ( n: integer :=3);
port (
  R : in std_logic_vector ( n downto 0) ;
  clk,reset,L: in std_logic;
  Q: out std_logic_vector ( n downto 0) );
```

```
end up_counter;
```

```
architecture arch of up_counter is
signal count : std_logic_vector( n downto 0);
begin
```

```
process ( clk,reset)
begin
if reset ='1' then
  count <=( others =>'0');
elsif rising_edge ( clk) then
  if L='1' then
    count<= R;
  else
    count <= count+1;
  end if;
```

```
end if;
end process;
Q<=count;
```

```
end arch;
```

# PARALLEL LOAD UP COUNTER (TEST BENCH)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity sim_counter is
generic ( n: integer:=3);
end sim_counter;

architecture Behavioral of sim_counter is
component up_counter is
generic ( n: integer :=3);
port (
    R : in std_logic_vector ( n downto 0) ;
    clk,reset,L: in std_logic;
    Q: out std_logic_vector ( n downto 0) );

end component;

signal R : std_logic_vector ( n downto 0) ;
    signal clk,reset,L: std_logic;
    signal Q: std_logic_vector ( n downto 0) ;
begin

U: up_counter
```

```
generic map ( n=>n)
port map ( R=>R, clk=>clk, reset => reset ,L=>L , Q =>Q);
```

```
process
begin
    clk<='0' ; wait for 5 ns;
    clk<='1' ; wait for 5 ns;
end process;
```

```
process
begin
    reset <='1' ; wait for 5 ns;
    reset <='0' ; wait ;
```

```
end process;
```

```
process
begin
    L <='0' ; wait for 20 ns;
    L <='1' ; wait for 15 ns ;
    L <= '0' ; wait ;
end process;
```

```
process
begin
    R <= "1010"; wait;
end process;
end Behavioral;
```



# MODULUS-10 UP COUNTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity n_bit_upcounter is
    generic ( n:integer:=3);
    Port ( clk : in STD_LOGIC;
          En : in STD_LOGIC;
          reset : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (n downto
0));
end n_bit_upcounter;
```


```
architecture Behavioral of
n_bit_upcounter is
    signal count : std_logic_vector ( n
downto 0);
begin
```

```
process ( reset,clk,En )
```


```
begin
    if reset ='1' then
        count<= (others=>'0');
    elsif rising_edge (clk) then
        if En ='1' then
            if count="1010" then
                count<= (others=>'0');
            else
                count <= count+1;
            end if;
        end if;
    end if;
end process;

Q<= count;


end Behavioral;
```

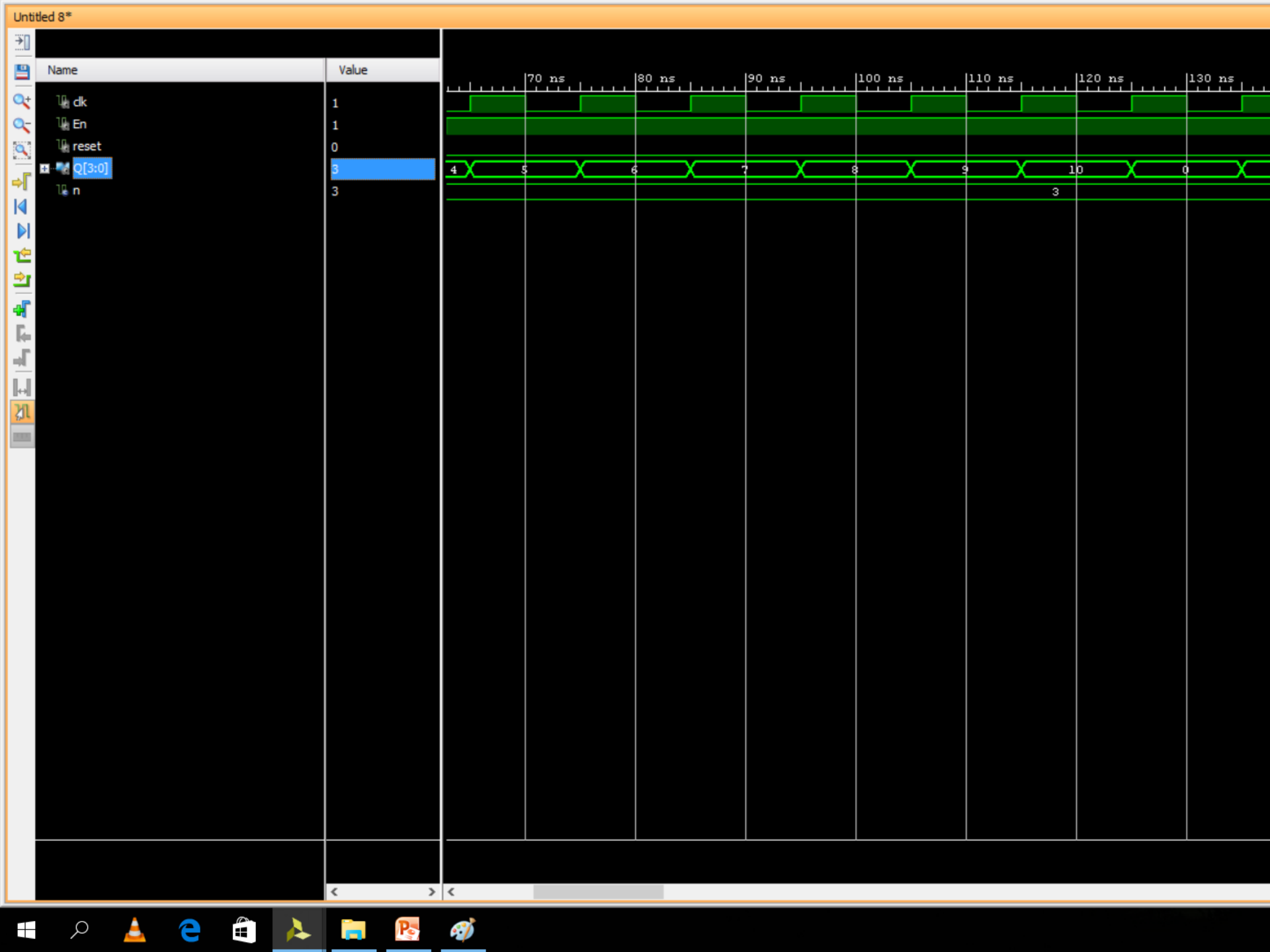




 

# CLOCK DIVIDER

 

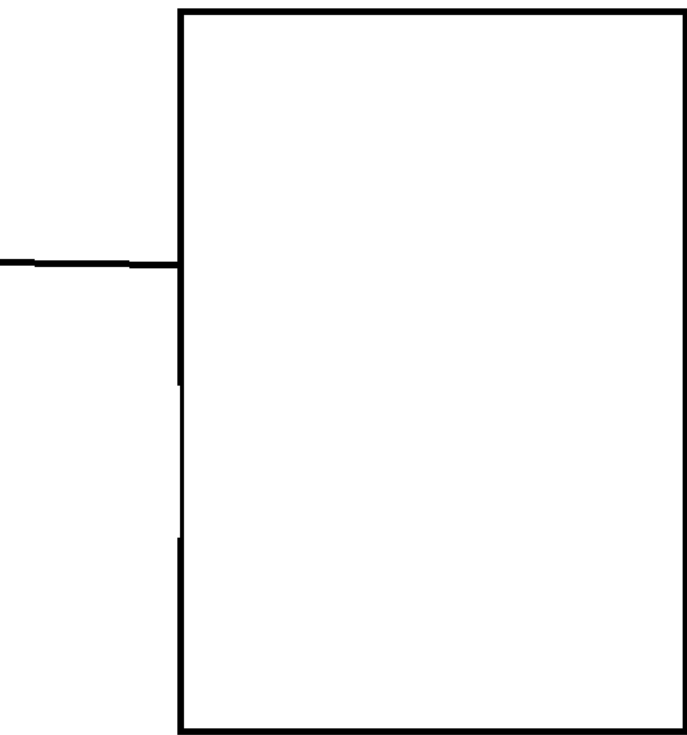


$$T = \frac{1}{10} = 100\text{ms}$$

clk\_100M

clk\_10

$$T = \frac{1}{100\text{M}}$$

 

$$100\text{M}/(10*2) - 1$$

,999,999

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity clk_divider is
    Port ( clk_100M : in STD_LOGIC;
           clk_10 : out STD_LOGIC);
end clk_divider;

```

```

architecture Behavioral of clk_divider is
    signal cnt:integer range 0 to 4999999:=0;
    signal clk1:std_logic:='0';
begin
    process ( clk_100M)

```

```

begin
    if rising_edge ( clk_100M) then
        if cnt = 4999999 then
            --( 100M/(10*2)-1)
            cnt <=0;
            clk1<= not clk1;
        else
            cnt <= cnt+1;
        end if;
    end if ;
end process;
clk_10 <= clk1;
end Behavioral;

```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.std_logic_unsigned.all;
```

```
entity sim is  
end sim;
```

```
architecture Behavioral of sim is
```

```
    component clk_divider is  
        Port ( clk_100M : in STD_LOGIC;  
              clk_10 : out STD_LOGIC);  
    end component;
```

```
    signal clk_100M:std_logic;
```

```
    signal clk_10: std_logic;
```

```
begin
```

```
    UU:clk_divider  
    port map  
    ( clk_100M => clk_100M ,  
      clk_10 => clk_10);
```

```
    process  
    begin  
        clk_100M <='0'; wait for 5 ns;  
        clk_100M <='1'; wait for 5 ns;  
    end process;
```

```
end Behavioral;
```

